

Procedure to find the region of operation in BJT

① Find $I_C(\text{sat})$ from the output loop (by making $V_{CE} = V_{CE}(\text{sat})$)

② Find
$$I_B(\text{min}) = \frac{I_C(\text{sat})}{\beta}$$

③ This is the minimum required current to drive the BJT into saturation.

④ From the input loop find the I_B

(a) If $I_B \leq 0 \rightarrow$ cut off region


(b) If $I_B \leq I_B(\text{min}) \rightarrow$ active region

(c) If $I_B \geq I_B(\text{min}) \rightarrow$ Saturation region

⑥

Assuming $V_{CE(sat)} = 0.2V$ and $\beta = 50$, the minimum base current (I_B) required to drive the tx in the given figure to saturation is

$$I_{B(min)} = \frac{I_C(sat)}{\beta}$$

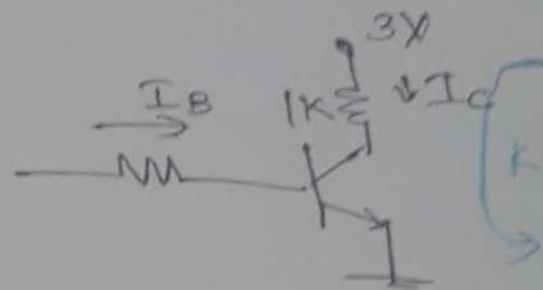

Step: 1

KVL \rightarrow

$$3 - I_C(sat) \times 1k - 0.2 = 0$$

$$I_C(sat) = \frac{3 - 0.2}{1k} = 2.8mA$$

$$\therefore I_{B(min)} = \frac{2.8mA}{50} = 56\mu A$$