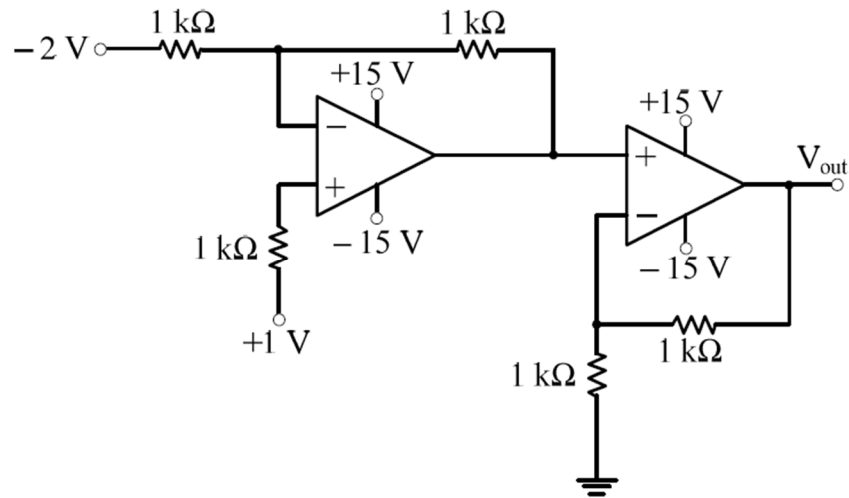


[Q] In the circuit shown below the op-amps are ideal. Then V_{out} in Volts is




(A) 4

(B) 6



(C) 8

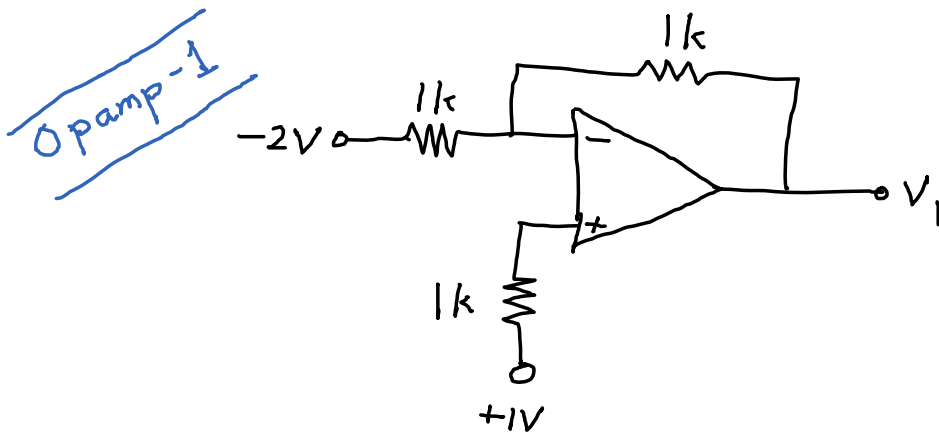(D) 10

Ans: Here, the output of the first op-amp is given as the input to the second op-amp. Considering the first op-amp alone



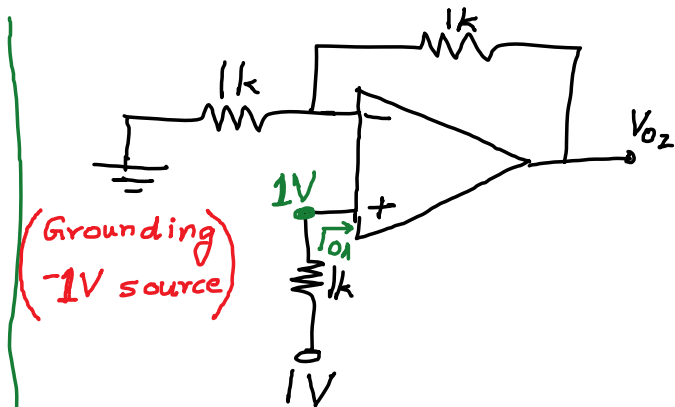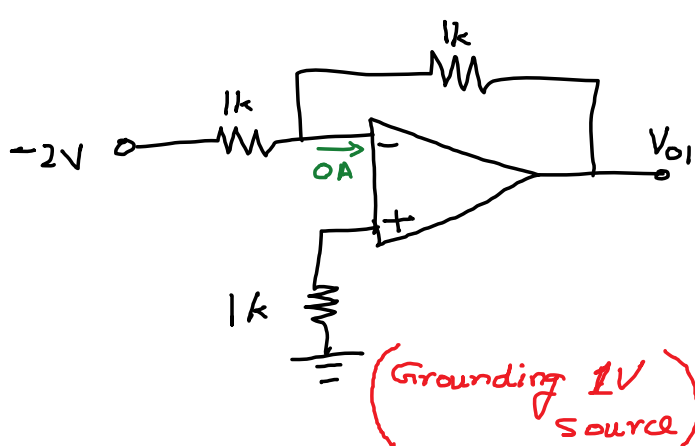Here V_1 can be found out using superposition theorem as:



$$V_{o1} = -2\left(\frac{-1k}{1k}\right) = 2V$$

(inverting configuration)


$$V_{o2} = 1\left[1 + \frac{1k}{1k}\right] = 2V$$

(noninverting configuration)

$$V_1 = V_{o1} + V_{o2} = 2V + 2V = \underline{\underline{4V}}$$

The input to the second op-amp is V_1


Opamp-2

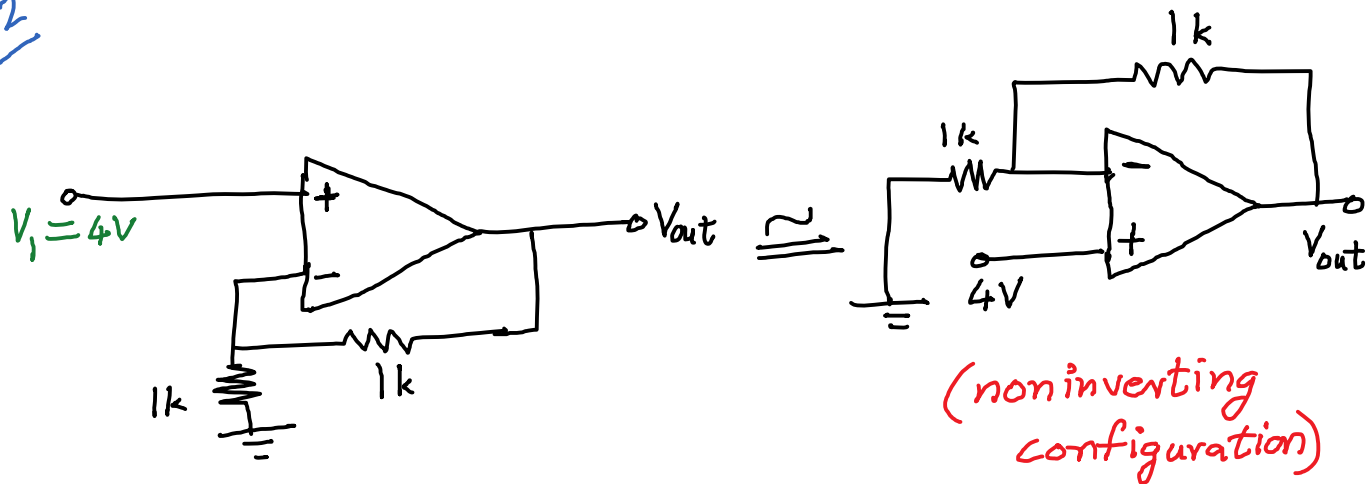


$$\therefore V_{out} = 4\left[1 + \frac{1}{1}\right] = \underline{\underline{8V}}$$

Answer: (C)

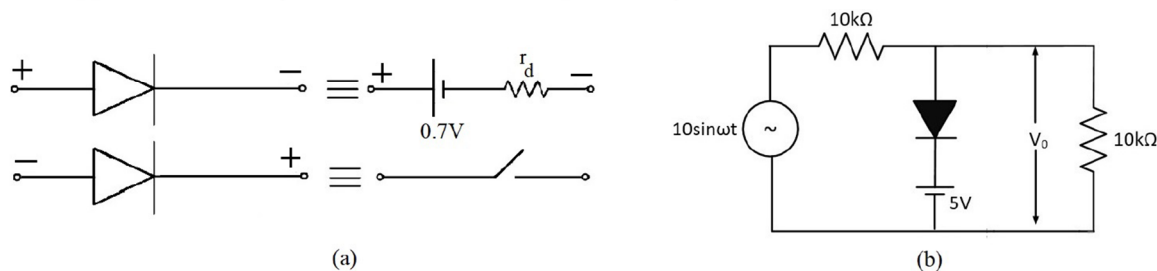
[Q] The equivalent circuits of a diode, during forward and reverse biased conditions are shown in figure (a). Here, r_d is the forward dynamic resistance of the diode. If such a diode is used in the clipper circuit of figure (b), sketch the output voltage (V_o).



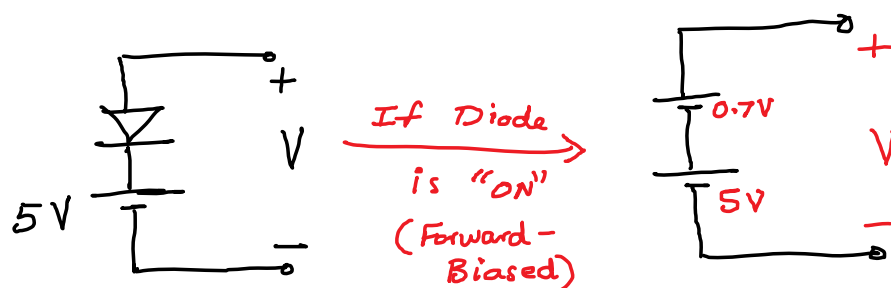Ans: Consider the diode along with 5V source together



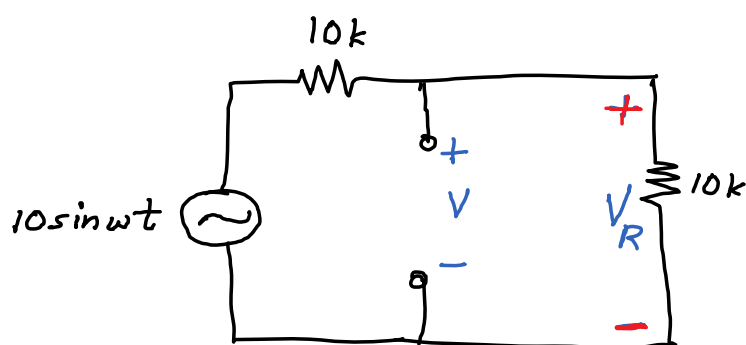From the figure, we know that for the Diode to be "ON", the voltage V must exceed $5.7V$ (to overcome the battery voltage $5V$ and diode forward voltage $0.7V$).



From the figure, we find that the voltage V (considered previously) is same as V_R .

$$\text{i.e., } V = V_R = V_{10k} = (10\sin\omega t) \times \frac{10k}{10k + 10k}$$

(voltage-division rule)


$$V = V_R = 10 \sin \omega t \times \frac{1}{2} = 5 \sin \omega t$$

$$V = V_R = 5 \sin \omega t \text{ — (1)}$$

i.e, the voltage V_R (across $10k\Omega$ resistor) as given in equation (1) must exceed $5.7V$ for the Diode to become "ON" (forward biased).

The maximum and minimum values of V are $+5V$ and $-5V$ respectively ($\because -1 \leq \sin \omega t \leq +1$)

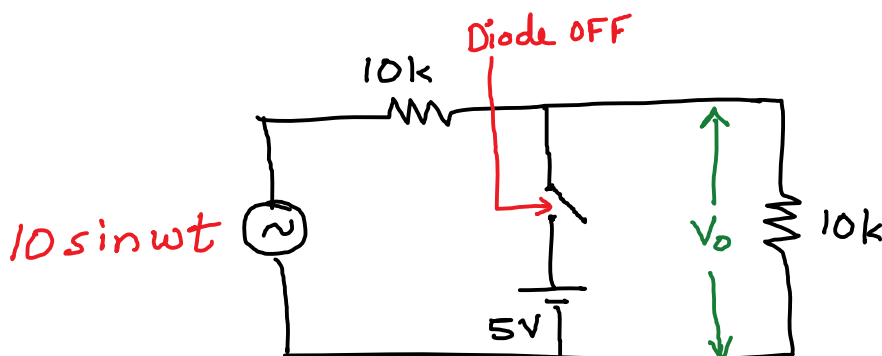Hence the diode never becomes "on" (forward biased).
The circuit may be redrawn as:



$\therefore V_o$ is given by

$$V_o = 10 \sin \omega t \times \frac{10k}{10k + 10k} = \underline{\underline{5 \sin \omega t}}$$

(voltage-division rule)

